

STUDENT ID NO

# **MULTIMEDIA UNIVERSITY**

# MODULE TEST 1

TRIMESTER 1, 2020/2021

### EEE 3156 DIGITAL SYSTEM

(EE Group)

26 AUGUST 2020

30 Minutes

#### INSTRUCTION TO STUDENT

- 1. This Question paper consists of 2 pages including cover page with 1 Question only.
- 2. Attempt **ALL** questions.
- 3. Please write all your answers on the Answer Sheet / Examination Pad / A4 paper.
- 4. Please write your student ID on every page of your answer sheet.
- 5. Please save your answer document in PDF format (Your Student ID-T1.pdf) and upload the document to Google classroom within 10 minutes after the end of the examination.

### **Module Test 1:**

(a) Compute the characteristic equation of function, F for the circuit shown in Figure Q1.

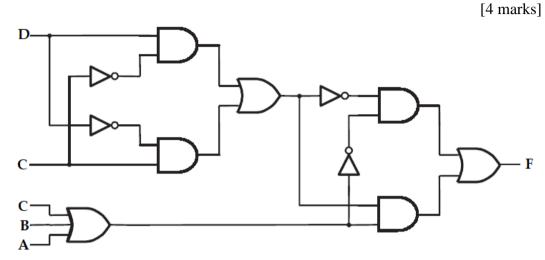


Figure Q1

(b) Construct the truth table of the circuit shown in Figure Q1.

[8 marks]

(c) Compute the simplified characteristic equation of function, F.

[4 marks]

(d) Design the function, F in part (c) using standard logic gates.

[6 marks]

(e) Design the function, F in part (c) using 4-input look up table.

[3 marks]

**End of Paper** 

PWL 2/2